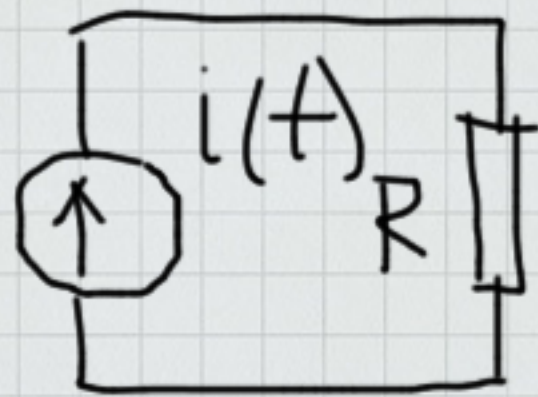



*Elektrik




$$v(t) = Ri(t)$$




tanpa inductan

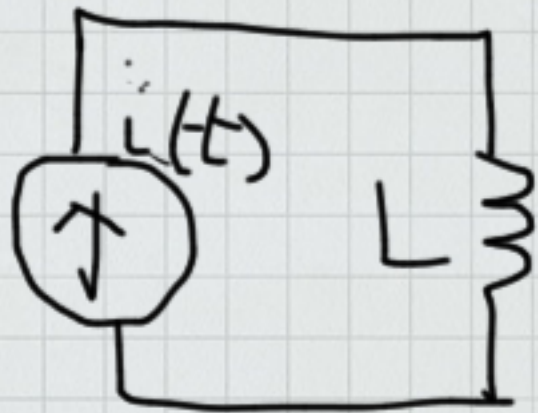

$$v(t) = L \frac{di(t)}{dt}$$

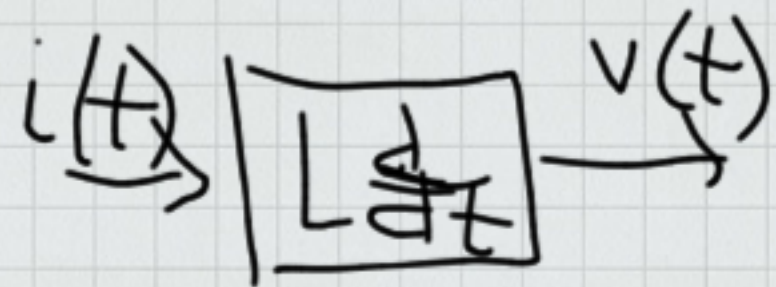

dengan inductan

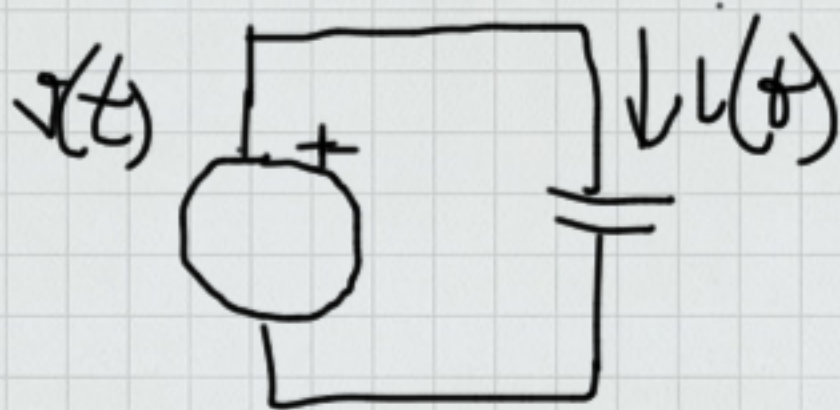

$$i(t) = C \frac{dv(t)}{dt}$$

