
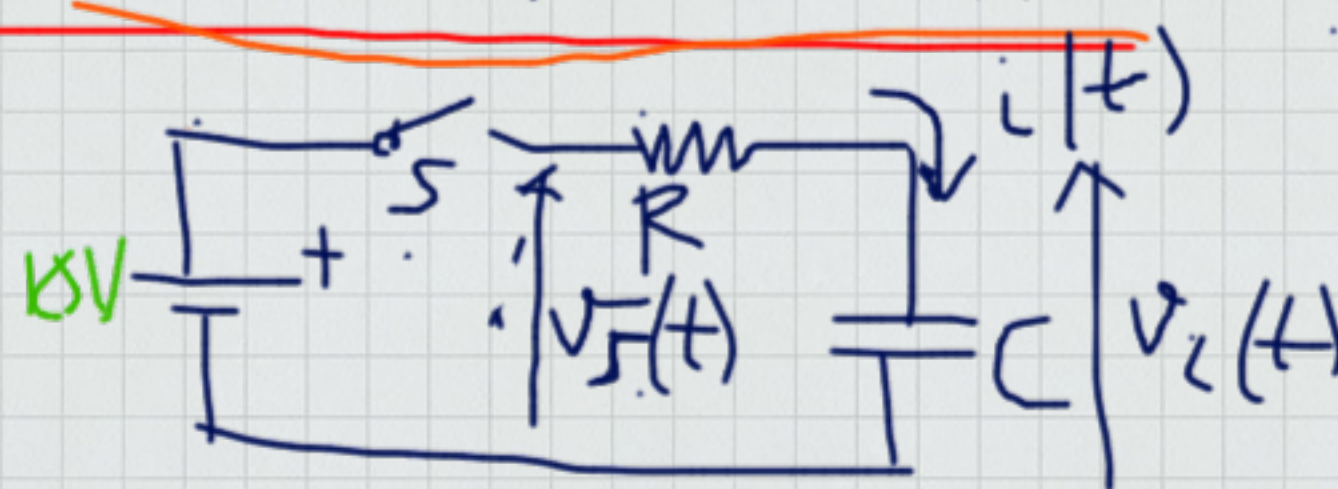


* Contoh Elektrik

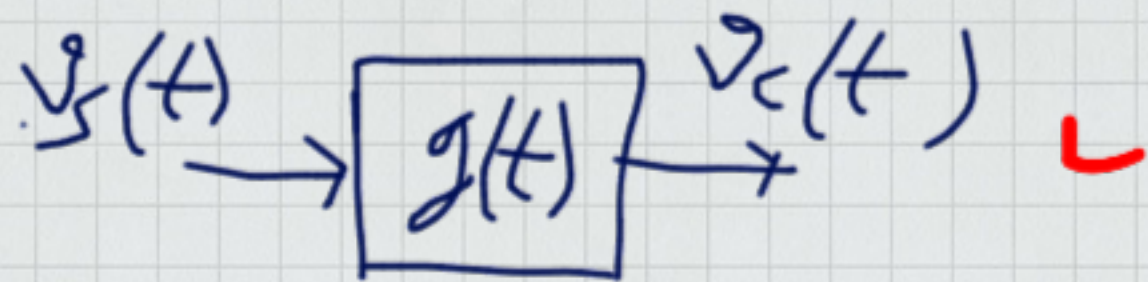

$t \leq 0$, C tidak bermuatan



Jika saklar S ditutup pada $t = 0$

* Aljabar bagan kotak

$$G(s) = \frac{V_c(s)}{V_s(s)}$$

* Transf. Laplace

* $V_s(s) = \dots$

* $V_c(s) = \dots$

* $V_c(t) = \mathcal{L}^{-1} V_c(s)$

