

$$V_c(s) = T(s) \cdot V_s(s) = \left(\frac{1}{RCs + 1} \right) \left(\frac{10}{s} \right) = \frac{10}{s(RCs + 1)}$$

Misalnya: $R = 100 \text{ k}\Omega$
 $C = 100 \mu\text{F}$ } $RC = 100 \times 10^3 \times 100 \times 10^{-6}$
 $\tau = 10 \text{ sec}$

$$* V_c(s) = \frac{10}{s(10s + 1)} = \frac{10}{s(\tau s + 1)} \quad \tau = \text{"tau" (time constant)}$$

$$* v_c(t) = \mathcal{L}^{-1} V_c(s) = \mathcal{L}^{-1} \frac{10}{s(10s + 1)}$$

$$= \mathcal{L}^{-1} \frac{\cancel{10}}{\cancel{10}s(s + 0.1)} = \mathcal{L}^{-1} \frac{1}{s(s + 0.1)}$$

$$\frac{1}{s(s + a)} = \frac{1}{a} (1 - e^{-at})$$

$$= \frac{1}{0.1} (1 - e^{-0.1t})$$