

Chart 8.1 CIRCUIT CONSTANTS OF SOME MAJOR PHASE CONTROLLED CIRCUITS†

(a) Name	(b) Connections	(c) Load voltage waveforms	(d) Peak forward voltage on SCR	Peak reverse voltage		(g) Max. load voltage ($\alpha = 0$) $E_D = \text{average d-c value}$ $E_a = \text{RMS a-c value}$
				(e) On SCR	(f) On diode	
(1) Half-wave resistive load			E	E	—	$E_D = \frac{E}{\pi}$ $E_a = \frac{E}{2}$
(2) Half-wave inductive load with free-wheeling rectifier			E	E	E	$E_D = \frac{E}{\pi}$
(3) Center-tap with resistive load, or inductive load with free-wheeling rectifier			E (possibly 2E if load open)	2E	E	$E_D = \frac{2E}{\pi}$
(4) Center-tap with resistive or inductive load—SCR in d-c circuit			E	0 ON CR ₁ ON CR ₂	$\frac{2E}{\pi}$	$E_D = \frac{2E}{\pi}$
(5) Center-tap with inductive load (no free-wheeling rectifier)			2E	2E	—	$E_D = \frac{2E}{\pi}$
(6) Single-phase bridge with 2 SCR's with common anode or cathode. Resistive load, or inductive load with free-wheeling rectifier			E	E (CR ₁ and CR ₂)	E	$E_D = \frac{2E}{\pi}$

† Assumes zero forward drop in semiconductors when conducting, and zero current when blocking; also zero a-c line and source reactance. Inductive d-c loads have pure d-c current.

Chart 8.1 (cont.)

(h) Load voltage vs trigger delay angle α	(i) Trigger angle full on to full off	Max. steady-state current in SCR		(m) Average amp	(n) Cond angle for max. current	(p) Ability to pumpback load energy to supply line	(q) Fundamental frequency of load voltage ($f = \text{supply frequency}$)	(r) Notes and comments
		(k) Average amp	(l) Cond. angle					
$E_D = \frac{E}{2\pi}(1 + \cos \alpha)$ $E_a = \frac{E}{2\sqrt{2}}(\pi - \alpha + \frac{1}{2} \sin 2\alpha)^{1/2}$	180°	$\frac{E}{\pi R}$	180°	—	—	—	f	
$E_D = \frac{E}{2\pi}(1 + \cos \alpha)$	180°	$\frac{E}{2\pi R}$ (load highly inductive)	180°	$0.54(\frac{E}{\pi R})$	210°	No	f	
$E_D = \frac{E}{\pi}(1 + \cos \alpha)$	180°	$\frac{E}{\pi R}$	180°	$0.26(\frac{2E}{\pi R})$	148°	No	2f	CR ₂ necessary when load is not purely resistive. Frequency limited by recovery characteristics of rectifiers and SCR.
$E_D = \frac{E}{\pi}(1 + \cos \alpha)$	180°	$\frac{2E}{\pi R}$	360°	$CR_1 = \frac{E}{\pi R}$ $CR_2 = 0.26(\frac{2E}{\pi R})$ with highly inductive load	180° 148°	No	2f	
$E_D = \frac{2E}{\pi} \cos \alpha$ (assuming continuous current in load)	180°	$\frac{E}{\pi R}$	180°	—	—	Yes	2f	
$E_D = \frac{E}{\pi}(1 + \cos \alpha)$	180°	$\frac{E}{\pi R}$	180°	$CR_1 = \frac{E}{\pi R}$ $CR_2 = 0.26(\frac{2E}{\pi R})$	180° 148°	No	2f	Without CR ₂ , SCR's may be unable to turn off on inductive load. Also, CR ₂ relieves SCR's from free-wheeling duty. See Sec. 5.5.