

Chart 8.1 (cont.)

(a) Name	(b) Connections	(c) Load voltage waveforms	(d) Peak forward voltage on SCR	Peak reverse voltage		(g) Max. load voltage ($\alpha = 0$) $E_D = \text{average d-c value}$ $E_D = \text{RMS a-c value}$
				(e) On SCR	(f) On diode	
(7) Single-phase bridge with 2 SCR's on common a-c line. Resistive or inductive load			E	E	E	$E_D = \frac{2E}{\pi}$
(8) Single-phase bridge with 4 SCR's and inductive load			E	E	$-$	$E_D = \frac{2E}{\pi}$
(9) Single-phase bridge with single SCR in d-c circuit. Resistive or inductive load			E	0	E (CR_1 and CR_2)	$E_D = \frac{2E}{\pi}$
(10) Three-phase half-wave with resistive load, or inductive load with free-wheeling rectifier			E (possibly $\sqrt{3}E$ if load open and if SCR's have high reverse currents)	$\sqrt{3}E$	E	$E_D = \frac{3\sqrt{3}E}{2\pi}$
(11) Three-phase half-wave with inductive load (no free-wheeling rectifier)			$\sqrt{3}E$	$\sqrt{3}E$	$-$	$E_D = \frac{3\sqrt{3}E}{2\pi}$
(12) Three-phase bridge with 3 SCR's. Resistive load, or inductive load with free-wheeling rectifier			$\sqrt{3}E$	$\sqrt{3}E$	$\sqrt{3}E$	$E_D = \frac{3\sqrt{3}E}{\pi}$
(13) Three-phase bridge with 6 SCR's. Resistive load, or inductive load with free-wheeling rectifier			$\sqrt{3}E$ (1.5E if SCR's shunted by resistance)	$\sqrt{3}E$	$\sqrt{3}E$	$E_D = \frac{3\sqrt{3}E}{\pi}$

Chart 8.1 (cont.)

(h) Load voltage vs trigger delay angle α	(i) Trigger angle range full on to full off	Max. steady-state current in SCR		Max. steady-state current in diode rectifier		(p) Ability to pumpback inductive load energy to supply line	(q) Fundamental frequency of load voltage ($f = \text{supply frequency}$)	(r) Notes and comments
		(k) Average amp	(l) Conduction angle	(m) Average amp	(n) Conduction angle for max. current			
$E_D = \frac{E}{\pi}(1 + \cos \alpha)$	180°	$\frac{E}{\pi}$	180°	$\frac{E}{\pi}$	180°	No	$2f$	Diode rectifiers act as free-wheeling path, conduct $(\pi + \alpha)$ degrees with inductive load.
$E_D = \frac{2E}{\pi} \cos \alpha$ (assuming continuous current in load)	180°	$\frac{E}{\pi}$	180°	$-$	$-$	Yes	$2f$	With resistive load operation is same as circuit (7).
$E_D = \frac{E}{\pi}(1 + \cos \alpha)$	180°	$\frac{2E}{\pi}$	360°	$CR_1 = \frac{E}{\pi R}$ $CR_2 = 0.16 \left(\frac{2E}{\pi R} \right)$	180° 148°	No	$2f$	CR_2 necessary when load is not purely resistive. Frequency limited by recovery characteristics of rectifiers and SCR's.
$E_D = \frac{3\sqrt{3}E}{2\pi} \cos \alpha$ ($0 < \alpha < 30^\circ$)	150°	$\frac{\sqrt{3}E}{2\pi}$	120°	$0.16 \left(\frac{3\sqrt{3}E}{2\pi R} \right)$	134°	No	$3f$	
$E_D = \frac{3E}{2\pi} [1 + \cos(\alpha + 30^\circ)]$ ($30^\circ < \alpha < 150^\circ$)	150°	$\frac{\sqrt{3}E}{2\pi}$	120°	$-$	$-$	Yes	$3f$	
$E_D = \frac{3\sqrt{3}E}{2\pi} \cos \alpha$ (assuming continuous current in load)	180°	$\frac{\sqrt{3}E}{\pi}$	120°	$CR_1 = \frac{\sqrt{3}E}{\pi R}$ $CR_2 = 0.14 \left(\frac{3\sqrt{3}E}{\pi R} \right)$	120° 132°	No	$3f$	Without CR_2 , SCR's may be unable to turn off on inductive load. Also, CR_2 relieves SCR's from free-wheeling duty.
$E_D = \frac{3\sqrt{3}E}{2\pi} (1 + \cos \alpha)$	120°	$\frac{\sqrt{3}E}{\pi}$	120°	$0.056 \left(\frac{3\sqrt{3}E}{\pi R} \right)$	212°	No	$6f$	SCR's require two gate signals 60° apart each cycle, alternately a gate signal duration $> 60^\circ$.