

$v_c(t) = \dots$ adalah SOLUSI Pers. Diffe-
 rential di atas, yaitu
 tegangan pada kapasitor
 C , $t \geq 0$ (setelah sa-
 klar S ditutup).
 ↓
 DICARI
 * Analitik
 * Simulink

$$v_c(t) = -RC \frac{dv(t)}{dt}$$

No. 5H

D42114 ABC
 D42114 DEF

$RC =$ [second]

Contoh: D42114011 → $R = 11 \text{ K}\Omega$
 D421122 → $C = 22 \mu\text{F}$ } $RC = 0,242 \text{ sec}$

R (Ohm, Ω) ω
 C (Farad)
 $R = \text{ABC Kiloohm}$
 $\text{K}\Omega = 10^3 \Omega$

$C = \text{DEF } \mu\text{F}$
 $\mu\text{F} = 10^{-6} \text{ F}$