
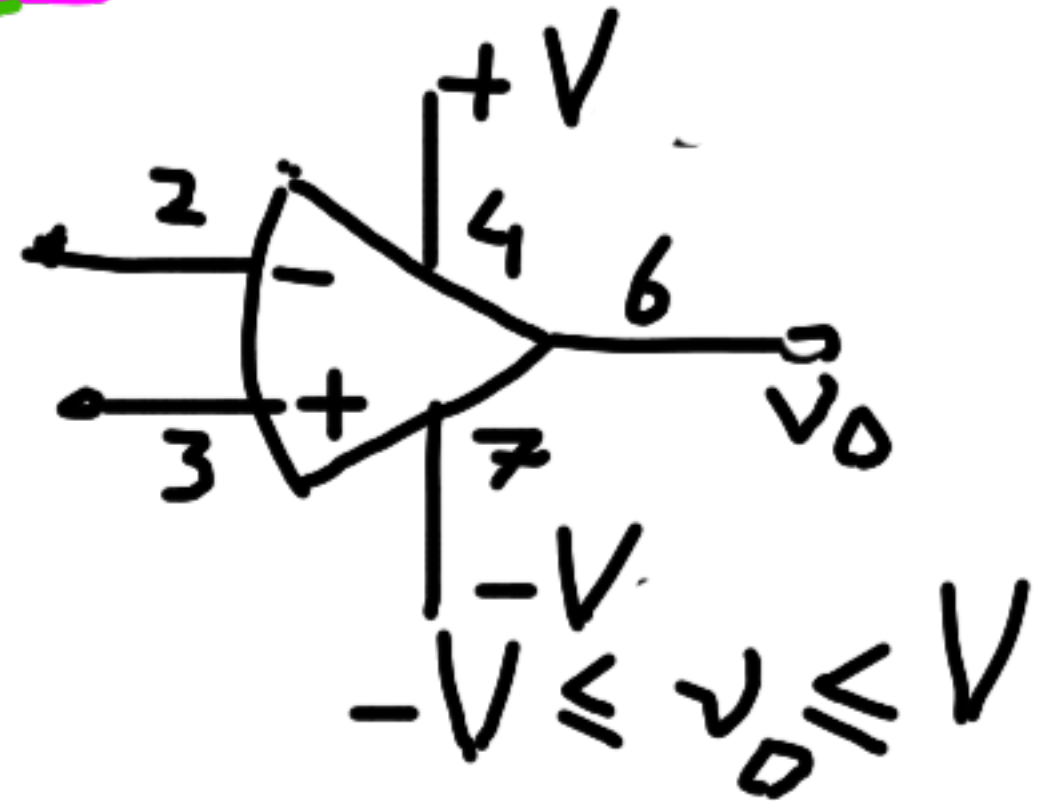


# RANGKAIAN OP-AMP

ideal

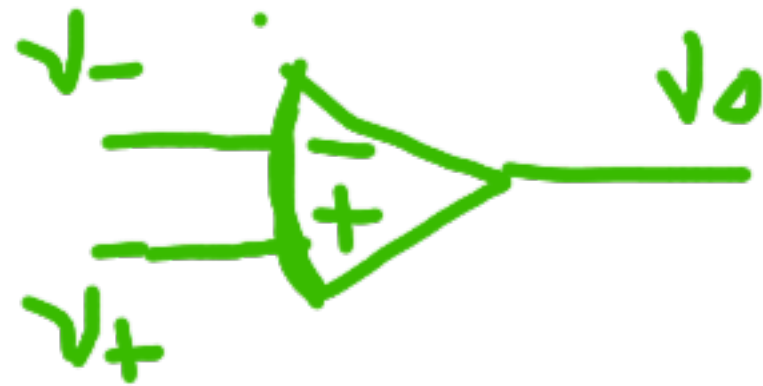

$v_-$  = inverting input  
 $v_+$  = non-inverting input  
 $v_0$  = keluaran (output)

4 karakteristik ideal

