

Para x_{art} $v_i(t) = +2 \rightarrow v_o(t) = -2,2 * 2 + 12,16$
 $= 7,76 > 5V$
 $= 5V$

$v_i(t) = -2 \rightarrow v_o(t) = -2,2 * (-2) + 12,16$
 $= 16,56 > 5V$
 $= 5V$

$v_i(t) = 0 \rightarrow v_o(t) = 12,16 > 5V$
 $= 5V$

