

Ketika  $v_+ < v_- = 0 \rightarrow v_o(t)$  jatuh ke  $-V$

$$\frac{R_1}{R_1 + R_2} v_i(t) + \frac{R_2}{R_1 + R_2} V < 0$$

$$R_1 v_i(t) + R_2 V < 0$$

$$v_i(t) < -\frac{R_2}{R_1} V$$

← LTP = Lower Trip Point

① Ketika  $v_i(t) \ll \text{negatif}$

$$v_+ < v_i \rightarrow v_o(t) = -V$$

Jika  $v_i(t)$  naik :  $I = \frac{v_i(t) - v_+}{R_2} = \frac{v_+ - (-V)}{R_1} = \frac{v_+ + V}{R_1}$

$$R_2 v_+ + R_2 V = R_1 v_i(t) - R_1 v_+$$

$$(R_1 + R_2) v_+ = R_1 v_i(t) - R_2 V \rightarrow v_+ = \frac{R_1}{R_1 + R_2} v_i(t) - \frac{R_2}{R_1 + R_2} V$$

Ketika  $v_+ > v_- = 0 \rightarrow v_o(t)$  naik ke  $+V$

$$R_1 v_i(t) - R_2 V > 0$$

$$v_i(t) > \frac{R_2}{R_1} V$$

→ UTP = Upper Trip Point