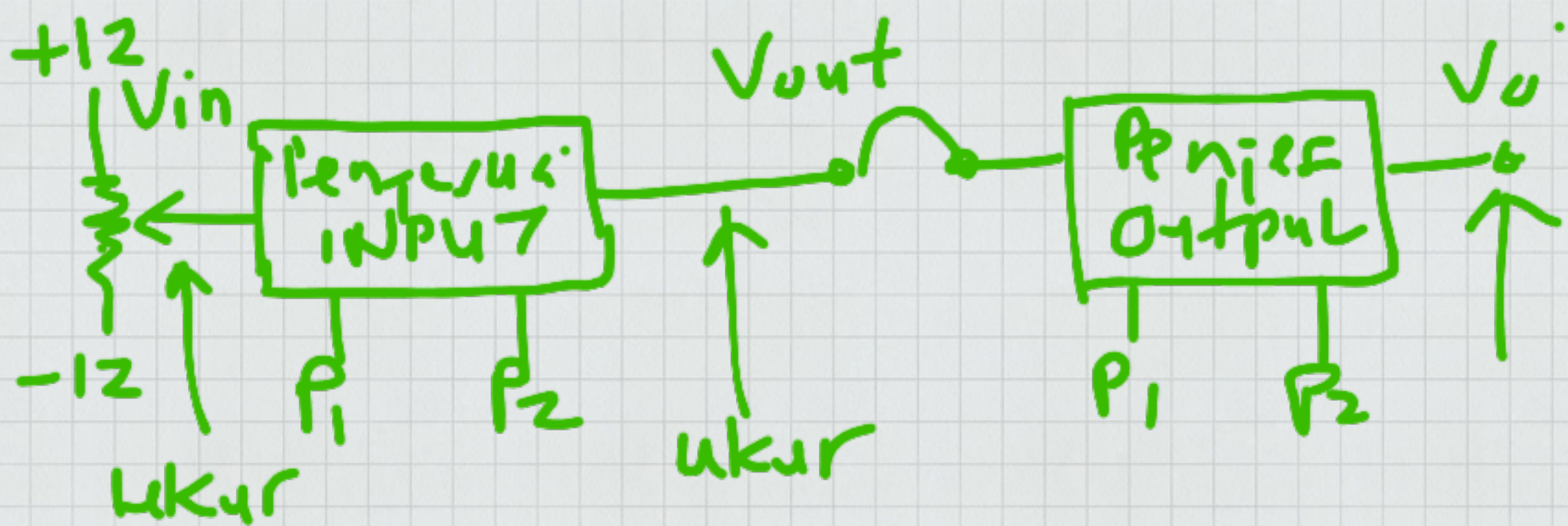




1. $V_{in} \rightarrow 0 \text{ Volt} \rightarrow V_{out} \rightarrow 1,5 \text{ Volt}$
Set P_2 pada penyesuaian output
 $V_o = 0 \text{ Volt}$
2. $V_{in} \rightarrow +12 \text{ Volt} \rightarrow V_{out} \rightarrow 3 \text{ Volt}$
Set P_1 pada penyesuaian output
 $V_o = +12 \text{ Volt}$
3. $V_{in} \rightarrow -12 \text{ Volt} \rightarrow V_{out} \rightarrow 0 \rightarrow V_o = -12 \text{ V.}$