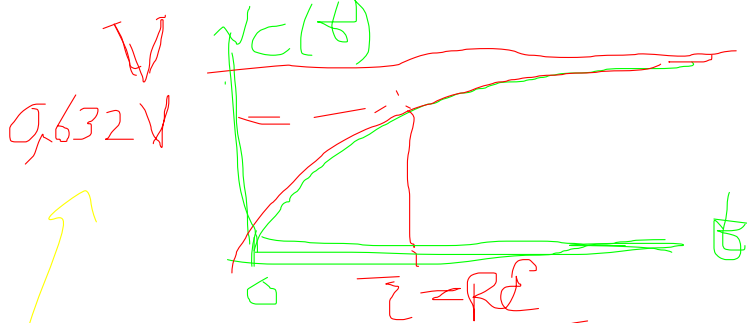




$$e^{-1} = 0,368$$

$$1 - e^{-1} = 0,632$$

konstanta waktu
 $\tau (\text{tau}) = RC$

$$V_c(s) = G(s) V_s(s)$$

$$= \left[\frac{1}{RCs + 1} \right] \frac{V}{s}$$

$$= \frac{V}{s(RCs + 1)}$$

$$= \frac{V}{RC} \left[\frac{1}{s(s + \frac{1}{RC})} \right]$$

$$V_c(t) = \mathcal{L}^{-1} \{ V_c(s) \}$$


$$= \frac{V}{RC} \mathcal{L}^{-1} \left\{ \frac{1}{s(s + \frac{1}{RC})} \right\}$$

$$= \frac{V}{RC} \left[RC(1 - e^{-t/RC}) \right]$$

hal. 362 App. baris 8



Analisis Transien

Contoh: Pemuatan Kapasitor

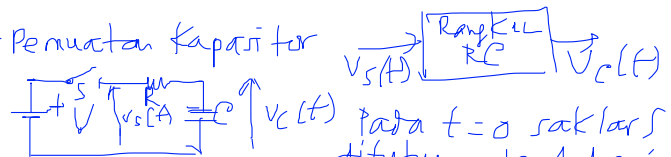

pada $t=0$ saklar ditutup tentukan:
 a) Model Nisbah Alih Rangkaian RC
 b) $V_c(t)$, $t \geq 0$

Konsep Impedansi

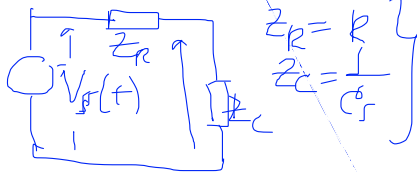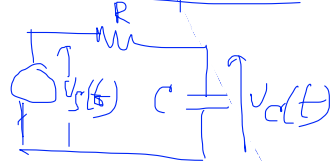

$$V_c(s) = \frac{Z_C}{Z_R + Z_C} V_s(s)$$

$$= \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} V_s(s)$$

$$= \frac{1}{RCs + 1} V_s(s)$$

a) Model Nisbah Alih



$$G(s) = \frac{V_c(s)}{V_s(s)} = \frac{1}{RCs + 1}$$

R [ohm] C [farad]
 $t \rightarrow$ [sec]

$$\tau = \frac{1}{RC}$$

b) $V_s(t) = V u(t)$

$$V_s(s) = V \int_0^\infty u(t) e^{-st} dt$$

$$= \frac{V}{s}$$

$u(t) = 1$ farat undak ratu
 $u(t) = \begin{cases} 0, & t < 0 \\ 1, & t \geq 0 \end{cases}$ (unit step)

$$V_c(t) = V(1 - e^{-t/RC})$$