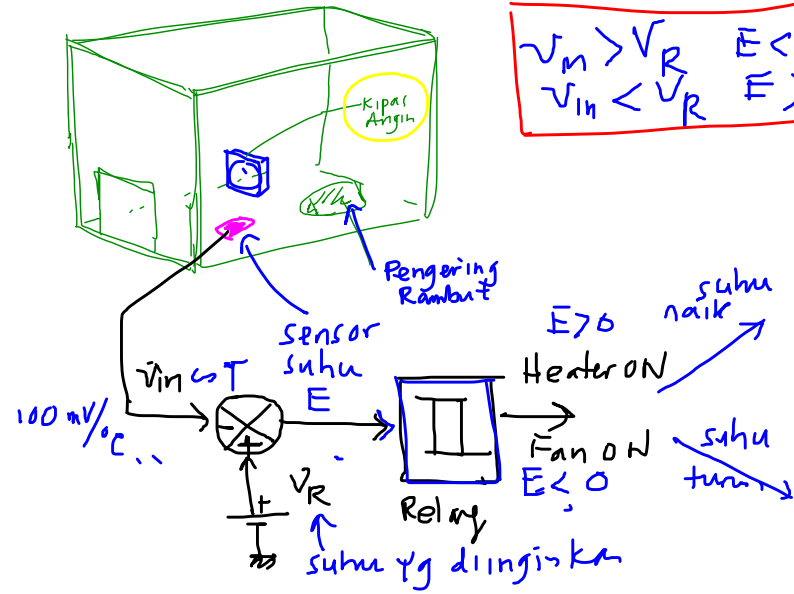


Project 4 PEMANAS RUANG



$$\begin{aligned} V_m > V_R & \quad E < 0 \quad \text{FAN ON} \\ V_m < V_R & \quad E > 0 \quad \text{Heater ON} \end{aligned}$$

Model Simulink:

